

GATE-BM2021-6

December 20, 2023

1. In the circuit shown below, Y is a 2-bit (Y_1Y_0) output of the combinational logic. What is the maximum value of Y for any given digital inputs, A_1A_0 and B_1B_0 ? (GATE-BM2021)

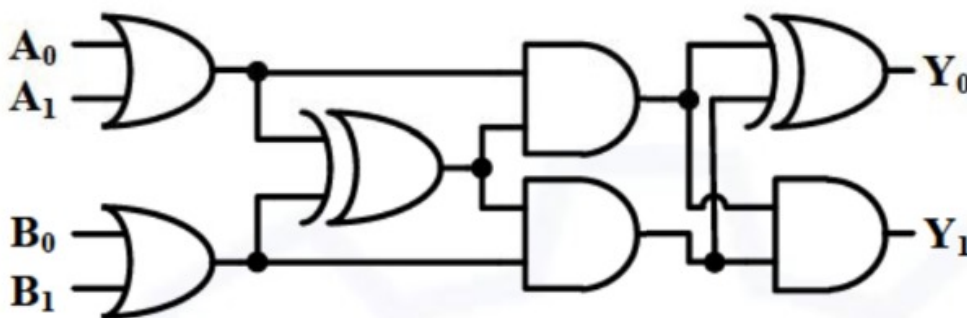


Figure 1:

- (A) 01
- (B) 10
- (C) 00
- (D) 11

()